



A-2991
Second Year B. Sc. (Sem. III) Examination
March/April – 2015
Electronics : Paper - IV
(Advance Digital Electronics & Circuit Design)

Time : 2 Hours]

[Total Marks : 50

Instructions :

(1)

<p>नीचे दर्शायेव निशानीवाणी विगतो उत्तरवही पर अवश्य कर्जवी. Fillup strictly the details of signs on your answer book.</p> <p>Name of the Examination : S. Y. B. SC. (SEM. 3)</p> <p>Name of the Subject : ELECTRONICS : PAPER - 4</p> <p>Subject Code No. : 2 9 9 1 Section No. (1, 2,.....): Nil</p>	<p>Seat No. : <input type="text"/><input type="text"/><input type="text"/><input type="text"/><input type="text"/><input type="text"/></p> <p style="text-align: center;">Student's Signature</p>
---	---

- (2) Figures on the right indicate full marks
- (3) All symbols and abbreviations have their usual meaning.
- (4) Non-programmable calculators are allowed.
- (5) Q.1 is compulsory.
- (6) Assume data if necessary.

- 1 Answer in short (4×2) : 8
- (a) State the main limitations of the S-R Flip Flop
 - (b) Compare RAM and ROM
 - (c) Why we use buffer register?
 - (d) State the various applications of the counters

- 2 (a) Draw the circuit diagram of D- Flip Flop and explain the truth table of it. 7
- (b) Explain the working of the clocked RS flip flop 7

OR

- (a) Explain how we use flip flop in register and explain Bidirectional register in brief. 7
- (b) Explain serial in, serial out Shift register with circuit diagram. 7

- 3 (a) Explain MOD-08 Counter in detail with all counting sequences. 7
- (b) Explain working of the Ripple Counter in detail. 7
- OR**
- (a) Explain working of 4-bit binary parallel adder in detail. 8
- (b) Discuss the working of Digital Comparator 6
- 4 Write Short Notes : (Any Two) 14
- (1) J –K Flip Flop
- (2) Semiconductor memory
- (3) Serial In Parallel Out Register
- (4) BCD adder.
-