



AB-3184

Third Year B.Sc. (Electronics) (Sem. V) Examination

March/April – 2015

Electronics : Paper - VI

(Theory of Operational amplifier)

Time : 2 Hours]

[Total Marks : 50

Instruction :

(1)

नीचे दृष्टावेक निशानीवाणी विगतो उत्तरवडी पर अवश्य लपवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
THIRD YEAR B.SC. (ELECTRONICS) (SEM. V)	<input type="text"/>
Name of the Subject :	<input type="text"/>
ELECTRONICS : PAPER - VI	<input type="text"/>
Subject Code No. : <input type="text" value="3"/> <input type="text" value="1"/> <input type="text" value="8"/> <input type="text" value="4"/>	<input type="text"/>
Section No. (1, 2,...): <input type="text" value="Nil"/>	
Student's Signature	

- (2) Figures on the right indicate full marks.
- (3) All symbols and abbreviations have their usual meaning.
- (4) Non-programmable calculators are allowed.
- (5) Q.1 is compulsory.
- (6) Assume data if necessary.

1 Answer in brief: 14

- (1) What are the different blocks of a feedback amp?
- (2) Define CMRR
- (3) What are the disadvantages of open loop op-amp configuration?
- (4) Draw the pin configuration of IC 741C
- (5) Enlist the characteristics of an ideal op-amp?
- (6) Why operational amplifier is called so?
- (7) What is voltage follower?

2 (a) Derive the expression for voltage gain and input resistance of inverting amplifier with feedback. 8

- (b) The 741C is configured as an inverting amplifier 4
with $R_1 = 1k\Omega$, $R_F = 10k\Omega$. Compute the closed loop voltage gain and input resistance.

OR

AB-3184]

1

[Contd...

2 (a) Find out the operating point of a dual input unbalanced output differential amplifier. 6

(b) Design a zener constant current bias circuit according to the following specifications: 6

Emitter current $I_{E3} = 4\text{mA}$. Zener diode with $V_Z = 3.9\text{V}$

and $I_{ZT} = 45\text{mA}$. Transistor with $\beta_{ac} = \beta_{dc} = 100$ and

$V_{BE} = 0.7\text{V}$ and supply voltage = $\pm 9\text{V}$.

3 (a) Explain peaking amplifier with a neat diagram and frequency response. 7

(b) For a peaking amplifier, $R_1 = 1\text{k}\Omega$, $L = 100\mu\text{H}$ with 3Ω 5

internal resistance, $C = 0.01\mu\text{F}$, $R_F = 6.8\text{k}\Omega$ and

$R_L = 10\text{k}\Omega$. Find out the peak frequency.

OR

(a) Explain summing and averaging amplifiers using op-amps (non-inverting configuration). 6

(b) The 741C op-amp is connected as a voltage follower. 6

Compute the values of A_F , R_{IF} , R_{OF} and f_F for it.

s

4 (a) Analyze a differential amplifier with one op-amp. Explain its disadvantages. 8

(b) In a differential amplifier with one op-amp, 4

$R_1 = R_2 = 1\text{k}\Omega$, $R_F = R_3 = 10\text{k}\Omega$. and the op-amp is 741C.

What are the gain and input resistance of the amplifier?

OR

(a) Explain how instrumentation amplifier is used as light intensity meter. 7

(b) Discuss a basic integrator circuit and its drawbacks. 5