



AC-1720

B. Sc. (IT) (Sem. - II) Examination

April / May - 2015

Electronics & Digital Communication

Time : 3 Hours]

[Total Marks : 70

Instruction :

नीचे दृशावेव निशानीवाणी विगतो उत्तरवही पर अवश्य लपवी.  
Fillup strictly the details of signs on your answer book.

Name of the Examination :  
B. Sc. (IT) (Sem. - II)

Name of the Subject :  
ELECTRONICS & DIGITAL COMMUNICATION

Subject Code No. : 1 7 2 0 Section No. (1, 2,.....): Nil

Seat No. :  
[ ] [ ] [ ] [ ] [ ] [ ]

Student's Signature

Q.1 (18)

Q.1 A) Answer the following short questions in one or two sentences. (Any Six) (06)

- 1) How many valance electrons in intrinsic semiconductor?
- 2) What is break over voltage in SCR?
- 3) What is impedance?
- 4) Write difference between variable resistor and Light dependant resistor.
- 5) Explain radiation transmission lose.
- 6) Write color band for 38700 ohm +/- 5% resistance value.
- 7) Calculate resistance values from color code of the resistance  
a. green, blue, orange, silver

Q.1 B) Answer the following questions in detail. (Any Two) (12)

- 1) a) Write short note on half-wave rectifier.  
b) Write short note on Transmitter.
- 2) Write short note on extrinsic semiconductor.
- 3) Explain Bipolar Junction Transistor (BJT) amplifier application with the help of necessary circuit diagram and graphs.

Q.2 (18)

Q.2 A) Answer the following questions in detail. (Any Six) (06)

- 1) Write Ohms law
- 2) What is full form of FSK?
- 3) List out active and passive electronic components.
- 4) \_\_\_\_\_ is measurement unit of resistor.
- 5) Write full form of IGFET.
- 6) \_\_\_\_\_ diode use in voltage regulator applications.
- 7) What is resonance frequency?

Q.2 B) Answer the following questions in detail. (Any Two) (12)

- 1) Write short note on centre taped full wave rectifier.
- 2) Describe different type of resistors. Explain color coding for resistance value with the help of color code table.
- 3) Write short note on serial R-L and R-C circuit.

**Q.3** (18)  
**Q.3 A) Answer the following questions in detail.** (06)

- 1) Write full form of SCR
- 2) Explain Difference between conductor and insulator.
- 3) List out different applications of LED.
- 4) \_\_\_\_\_ are minority charge carrier in P-type semiconductor.
- 5) List out different transmission losses.
- 6) List out different advantages of JFET

**Q.3 B) Answer the following questions in detail. (Any Two)** (12)

- 1) a) Write short note on Kirchhoff's Voltage law (KVL).  
b) Write short note on Thevenin's theorem.
- 2) Write short note on Amplitude modulation.
- 3) Explain internal construction of DE-MOSFET and its operation with the help of characteristics.

**Q.4** (16)

**Q.4 find out true or false from given statements** (04)

- 1) JFET is Unipolar device.
- 2) SCR three terminal names are Anode, Cathode and Gate.
- 3) Watt is the measurement unit of power.
- 4) TESLA is the unit of current.

**Q.4 Answer the following questions in detail. (Any Two)** (12)

- 1) Explain internal construction of P-N junction diode. Draw diode output characteristic graph and explain reverse biased operation.
- 2) Write short note on ASK and FSK.
- 3) Write short note on filter.