



**AC-3309**  
**First Year B. Sc. (Sem. II) Examination**  
**March/April – 2015**  
**Electronics : Paper - II**  
*(Old Course) (Digital Electronic Circuits)*

Time : Hours]

[Total Marks : 50

**Instructions : (1)**

<p>नीचे दृष्टावेक निशानीवाणी विगतो उत्तरवडी पर अवश्य लपवी. Fillup strictly the details of signs on your answer book.</p> <p>Name of the Examination : <b>FIRST YEAR B. SC. (SEM. II)</b></p> <p>Name of the Subject : <b>ELECTRONICS : PAPER - II (OLD)</b></p> <p>Subject Code No. : <b>3 3 0 9</b> Section No. (1, 2,.....): <b>Nil</b></p>	<p>Seat No. : <input type="text"/><input type="text"/><input type="text"/><input type="text"/><input type="text"/><input type="text"/></p> <div style="border: 1px solid black; border-radius: 15px; padding: 10px; text-align: center; width: 100%;">Student's Signature</div>
---	---

- (2) Figures to right indicate full marks.  
(3) Q.1 is compulsory.

- 1 Answer in brief : 8
- (a) By how many variables the expression will be reduced in case of Quad and Octet in K-map.
- (b) Draw the truth table of 3-input XNOR gate.
- (c) What do you mean by "Don't care condition" ?
- (d) Convert Gray code 1011010111 to its Binary equivalent.
- 2 (a) Design and implement Binary to BCD code converter. 8
- (b) Design and implement Half and Full subtractor. 6
- OR
- 2 (a) Discuss, in detail, all the Boolean laws that are used for simplification of Boolean expression. 8
- (b) With suitable example, explain Hamming code in error detecting and correction. 6
- 3 (a) Design and implement Binary to Gray code converter. 8
- (b) Prove NAND and NOR as a Universal Logic gates. 6
- OR

- 3 (a) Perform the following : 8
- (i)  $23789_{10} = \text{_____}_2 = \text{_____}_8 = \text{_____}_{16}$
- (ii) Add  $(1101011011011_2)$  and  $(110010110111_2)$
- (b) Discuss the weighted and non-weighted codes. 6
- 4 Write short notes : (any two) 14
- (a) Applications of XOR and XNOR gate.
- (b) Error detecting and correcting codes.
- (c) Multiplexer and Demultiplexer
- (d) Excess-3 and BCD codes.
-