



DMM-3061

Second Year B. Sc. (Sem. IV) Examination

March / April - 2016

Electronics : Paper - III

Time : Hours]

[Total Marks : 50

Instructions :

(1)

नीचे दर्शायेव निशानीवाणी विगतो उत्तरवडी पर अवश्य वपनी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<input type="text" value="SECOND YEAR B. SC. (SEM. 4)"/>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<input type="text" value="ELECTRONICS : PAPER - 3"/>	<input type="text"/>
Subject Code No. : <input type="text" value="3"/> <input type="text" value="0"/> <input type="text" value="6"/> <input type="text" value="1"/>	<input type="text"/>
Section No. (1, 2,.....): <input type="text" value="Nil"/>	<input type="text"/>
	Student's Signature

- (2) Q. 1 is compulsory.
- (3) Figures at extreme right indicate full marks.
- (4) Draw figures/diagrams to support your answer.
- (5) Assume data, if required.

- | | | |
|---|---|---|
| 1 | Answer in Brief : | 8 |
| | (A) Classify the oscillator | |
| | (B) What do you mean by harmonic distortion in amplifier? | |
| | (C) What is tuned amplifier? | |
| | (D) What is cross over distortion? | |
| 2 | (A) Explain circuit and working of phase shift Oscillator | 8 |
| | (B) What are the basic conditions for the oscillation ? | 3 |
| | (C) Colpitt's oscillator if $L = 120\mu H$ $C_1 = 300pF$ $C_2 = 1200pF$. | 3 |
| | Find the frequency of oscillation | |

OR

- | | | |
|---|--|---|
| 2 | (A) Explain circuit and working of Bistable multivibrator | 8 |
| | (B) Explain general concept of transistor as switch | 3 |
| | (C) In Astable multivibrator $R_1 = R_2 = 10K\Omega$ $C_1 = C_2 = 0.01\mu F$ | 3 |
| | and $RL_1 = RL_2 = 1K\Omega$ find the minimum value of | |
| | transistor β . | |

- 3 (A) Explain Class B push pull amplifier with figure. 8
- (B) What are the basic differences between the voltage and power amplifier 3
- (C) A Class B push pull amplifier must deliver 10 W of audio - power to the out put load if the output transformer is 80% efficient. What is the max. power drain on the power supply under optimum conditions ? 3
- OR**
- 3 (A) Explain Single Input unbalanced Output Differential Amplifier with figure 8
- (B) Explain the basic concept of differential amplifier in detail 6
- 4 Write Short Notes : (Any Two) 14
- (A) Wein Bridge Oscillator
- (B) Astable Multivibrator
- (C) Class AB Push Pull Amplifier
- (D) Double Tuned Amplifier.
-