



RAN-1013

T.Y.B.Sc (PHYSICS) SEM: V (ID.) Examination

March / April - 2019

General Elective- Electronics (Can)

(Old or New to be mentioned where necessary)

[Total Marks: 50

सूचना : / Instructions

(1)

नीचे दृशविले निशानीवाणी विगतो उत्तरवली पर अवश्य लपववी.

Fill up strictly the details of signs on your answer book

Name of the Examination:

T.Y.B.Sc (PHYSICS) SEM: V (ID.)

Name of the Subject :

General Elective- Electronics (Can)

Subject Code No.: 1 0 1 3

Seat No.:

--	--	--	--	--	--

Student's Signature

- (2) The Marks shown on right is the full marks of Question.
(3) The symbols used in the question paper have their usual meaning.

Q-1 Give short answer of the following.

8

- 1 When the maximum power is transferred?
- 2 The energy of wave is directly proportional to its _____ .
- 3 A differential amplifier does not amplify _____ signals.
- 4 Modulation factor m is the ratio of _____ .
- 5 Side band power depends upon the _____ . (m , f_c , f_s).
- 6 A differential amplifier is sometimes called _____ .
[A] short-tail pair [B] long - tail pair
[C] open-tail pair [D] close-tail pair

- 7 Write the conditions to find d.c. equivalent circuit for transistor amplifier circuit.
- 8 What is the ideal value of CMRR?

Q.2 A For CE transistor amplifier circuit, explain phase reversal process at the collector w.r.t. input signal at base. Also explain it with graphical demonstration. **10**

OR

A Draw the circuit diagram of a two-stage RC coupled transistor amplifier. Explain the working and operation of the circuit in detail. Explain the frequency response and disadvantages. **10**

B If the overall gain of the two-stage RC coupled transistor amplifier is 80 dB and the voltage gain of second stage is 150, calculate the voltage gain of first stage in dB. **4**

OR

B Determine the transformer turn ratio for transforming maximum, power to 10Ω load from source that has, output impedance of $1k\Omega$. Also calculate the voltage across the external load if the terminal voltage is $10 V_{rms}$. **4**

Q.3 A Explain differential amplifier. Explain working of differential inputs to get differential output. **10**

Explain **non inverting** input with differential type output and single ended type output.

Explain **inverting** input with differential type output and single ended type output.


OR

A Explain AC analysis of differential amp. for non inverting input, single ended output. Derive the equation for voltage gain. **10**

B Explain common mode gain and CMRR. **4**

OR

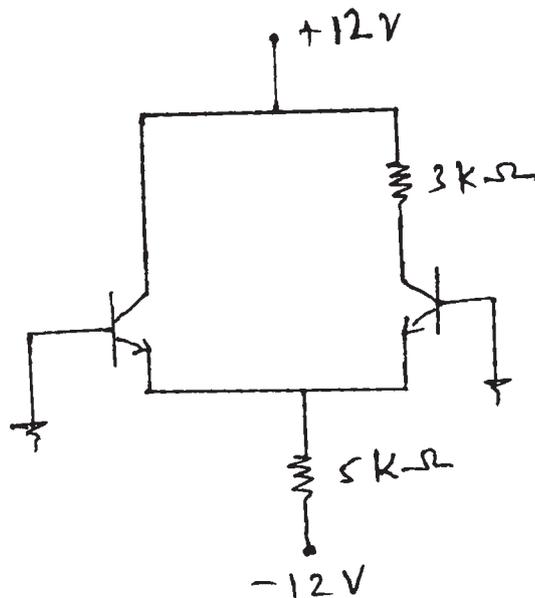B What are the currents and voltages in the single ended output circuit. Ignore V_{BE} . **4**



Q.4 A What is AM? With analysis of AM wave, show that AM wave contains three frequencies viz. f_c , f_c+f_s and f_c-f_s . Write down important points. **10**

OR

A Explain the power in AM wave, deriving the necessary equations. Explain limitations of Amplitude Modulation. **10**

B A carrier of 140V and 320 kHz is modulated by 70V, 300 Hz sine wave 4 signal. Find modulation index, side-band frequencies and bandwidth.

OR

B A 50 kW carrier wave is to be modulated to a level of (i)80% and (ii)10%. What is the total sideband power in each case? **4**
