



AC-1428

M. Sc. (Electronics) (Sem. II) Examination

April / May - 2015

EL - 422 : Op. Amp & Integrated Circuit Designing

Time : 3 Hours]

[Total Marks : 70

Instructions :

(1)

नीचे दशांशवैक निशानीवाणी विगतो उत्तरवडी पर अवश्य लपवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<input type="text" value="M. SC. (ELECTRONICS) (SEM. II)"/>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<input type="text" value="EL - 422 : OP. AMP & INTEGRATED CIRCUIT DESIGNING"/>	<input type="text"/>
Subject Code No. : <input type="text" value="1"/> <input type="text" value="4"/> <input type="text" value="2"/> <input type="text" value="8"/>	<input type="text"/>
Section No. (1, 2,.....): <input type="text" value="Nil"/>	<input type="text"/>
	Student's Signature

- (2) This question paper includes **Five** main questions with three sub-question (a), (b) and (c) in each.
- (3) Answer any **two** sub-questions form **each** main question.
- (4) Assume data if require.
- (5) Symbols used have their usual meaning.

- 1(a) With circuit diagram and mathematical formulas, describe operation of an Averaging Amplifier in inverting configuration. [7]
- (b) Using floating load type Voltage – to – Current converter, design 0V – to – 10V Volt-Meter (Assume that the meter movement requires 2 mA Current for its full scale deflection) and explain its working. [7]
- (c) What is the key difference between an instrumentation amplifier and an ordinary operational amplifier? Design an instrumentation amplifier with three Operational Amplifiers and explain its working. [7]
- 2(a) What is the difference between active and passive filters? Sketch the circuit diagram of a first order High-Pass filter and derive formula for its gain in terms of input frequency f , higher cut-off frequency f_H , and amplifier gain A_F . [7]
- (b) Using an Operational Amplifier, design first order Band – Pass active filter with frequency band of 20 Hz to 20 kHz and pass band gain of 4. [7]
- (c) With circuit diagram explain any one application of an active narrow band-pass filter. [7]

- 3(b) Sketch circuit diagram of an Operational Amplifier based Phase shift oscillator and with necessary formula explain its working. [7]
- (b) What is window detector? Design a window detector that gives positive output voltage only when its input is between 2 Volt and 5 Volts. [7]
- (c) With circuit diagram and formula, explain any one application of a Zero-Crossing detector. [7]
- 4(a) With necessary circuit diagram and mathematical formula, explain any one application of PLL. [7]
- (b) Sketch block diagram of Timer IC 555 and explain its application as an astable-multivibrator. [7]
- (c) What is a “Three pin” voltage regulator? Design a DC to DC converter that converts -9.0 Volts to -6.0 Volts three pin regulator and explain its working. [7]
- 5(a) Why Power Amplifiers are required? Draw the circuit diagram of LM 380 based power amplifier and explain its working. [7]
- (b) Using IC LM 317, design an adjustable positive voltage regulator to satisfy following specifications. [7]
- Output Voltage = 3 to 9 Volt and
Output current = 1 Amp.
- Also calculate the minimum input voltage required.
- (c) Sketch an internal functional block diagram and with formula and external circuit components, explain working of an IC 8038 function generator. [7]
-