



AC-1586
M. Sc. (Sem. IV) Examination
April / May – 2015
Electronics : CEL - 543
(Analog & Digital Circuits)

Time : 3 Hours]

[Total Marks : 70

Instructions :

(1)

<p>नीचे दशांशके निशानीवाणी विगतो उत्तरवही पर अवश्य लखवी. Fillup strictly the details of signs on your answer book.</p> <p>Name of the Examination : M. SC. (SEM. 4)</p> <p>Name of the Subject : ELECTRONICS : CEL - 543</p> <p>Subject Code No. : 1 5 8 6 Section No. (1, 2,.....): Nil</p>	<p>Seat No. : □ □ □ □ □ □</p> <p style="text-align: center; border: 1px solid black; border-radius: 15px; padding: 10px;">Student's Signature</p>
--	---

- (2) Figures to the right hand side indicate full marks.
- (3) Assume data if required.
- (4) Symbols have their usual meaning.
- (5) Simple calculator is allowed to use.

1 Attempt any two:

- (a) Sketch the diagram of MOSFET and explain its working in the enhancement mode. Also derive the equation for its volt-ampere characteristics. 7
- (b) Describe the working and application of CMOS devices with the help of suitable example. 7
- (c) What are dynamic MOS Shift registers? Explain the working of NMOS dynamic shift register with the help of a suitable block diagram and truth table mention the applications of these registers. 7

2 Attempt any two :

- (a) Describe the use of VLSI planner process to prepare and integrate a FET on a silicon chip. 7

- (b) Describe how will you prepare the following components 7
- (i) IC resistors
 - (ii) IC capacitors
- (c) (i) Write a note on integrated circuit packaging. 3
- (ii) What is the total length required to fabricate 25 k.ohm register whose width is $25\mu\text{m}$. If $R_s=200\text{ ohm/square}$. 4
- 3** Attempt any two:
- (a) Explain why the quiescent collector current must be essentially independent of variations in B_F to achieve bias stabilization. Derive the formula for IC dependence on B_F , V_{BE} and I_{CO} . 7
- (b) (i) What is meant by zero frequency resistance R_{ii}^0 ? 3
- (ii) Explain pole-zero method for amplifier having two poles in detail. 4
- (c) (i) Explain dominant pole method explain its significance for high frequency response. 3
- (ii) (a) For the Widlar circuit, determine R so that $I_C = 1\text{ mA}$. The transistor parameters are $V_{BE}=0.7\text{ V}$, $B_F=100$ and an infinite Early voltage is assumed. The supply voltage is 15V . 3
 - (b) For R obtained in part (a), determine the present change in I_C for $B_F = 200$. 4
- 4** Attempt any two:
- (a) Explain the following terms: 7
- (i) Multiloop feedback amplifier.
 - (ii) Stability
 - (iii) open loop poles.
- (b) Explain test for stability with Nyquist's criterion. 7
- Comment on your result.
- (c) What is 't' model, Derive equations for t parameters in terms of x_i, \hat{x}_i, x_s and x_o . 7

- 5** Attempt any two :
- (a) Draw an ideal characteristic of an Inverter. **7**
How such characteristics are possible in NMOS technology. Explain such circuit in detail.
 - (b) List the limitations of PROM. Explain their **7**
operation with detail architecture.
 - (c) (i) Explain PLA or PAL. **3**
(ii) Consider a 4kb ROM with 4 output bits. If **4**
the encoder is square, how many bits are needed
for x address.
-