

- 1 Power gain is always
 - (A) A negative number
 - (B) Zero
 - (C) All these
 - (D) A positive number

- 2 Input resistance for CC amplifier is
 - (A) Low
 - (B) Zero
 - (C) None of these
 - (D) High

- 3 The function of a transistor is to do _____.
 - (A) Amplification
 - (B) Filtering
 - (C) Regulation
 - (D) Rectification

- 4 Stabilization means making _____ independent of temperature variations or variations of transistor parameters.
 - (A) Supply Voltage
 - (B) Input Current
 - (C) Collector Current
 - (D) Operating Point

- 5 Which circuit has highest stability factor ?
- (A) Emitter bias circuit
 - (B) Collector to base bias circuit
 - (C) Voltage divider bias with emitter bias
 - (D) Fixed bias circuit
- 6 In the low frequency region of RC coupled amplifier the effect of capacitance is such that
- (A) Shunt capacitors are opened
 - (B) The series capacitors and shunt capacitors are opened
 - (C) The series capacitors and shunt capacitors are shorted
 - (D) The series capacitors are shorted
- 7 The half power frequency is also known as
- (A) Corner frequency
 - (B) Break frequency
 - (C) All of these
 - (D) Cut off frequency
- 8 What is the phase difference between input voltage and output voltage in a common emitter amplifier ?
- (A) -180°
 - (B) 0
 - (C) 90°
 - (D) 180°

- 9 For proper operation to transistor as an amplifier, (CE configuration) base emitter junction should be _____ and collector emitter junction should be _____.
- (A) (forward biased, reverse biased)
 - (B) (forward biased, forward biased)
 - (C) (reverse biased, reverse biased)
 - (D) (reverse biased, forward biased)
- 10 What is the main advantage of CE amplifier over CB amplifier as far as biasing is concerned ?
- (A) Small input resistance
 - (B) Less voltage gain
 - (C) None of these
 - (D) Single battery operation
- 11 Which circuit is the best biasing circuit ?
- (A) Emitter bias circuit
 - (B) Collector to base bias circuit
 - (C) Voltage divider bias with emitter bias
 - (D) Fixed bias circuit
- 12 Input resistance for CB amplifier is
- (A) Less than h_{ib}
 - (B) Equal to h_{ib}
 - (C) Greater than h_{ie}
 - (D) Greater than h_{ib}

- 13 An amplifier has a voltage gain of 100. What will be the voltage gain if 10% negative feedback is given ?
- (A) 90%
 - (B) 90.0
 - (C) 0.909
 - (D) 9.09
- 14 An amplifier has a voltage gain of 40 and 200 kHz bandwidth. Calculate the bandwidth with feedback if a 10% negative feedback is introduced in series with input.
- (A) 10 kHz
 - (B) 1000 kHz
 - (C) 500 kHz
 - (D) 100 kHz
- 15 Example of voltage series negative feedback amplifier is
- (A) CE amplifier without bypass capacitor
 - (B) CC amplifier
 - (C) CB amplifier
 - (D) CE amplifier with bypass capacitor
- 16 The circuit which exhibits 100% negative feedback
- (A) CE amplifier without bypass capacitor
 - (B) Collector to base biasing circuit
 - (C) Emitter follower
 - (D) CE amplifier with bypass capacitor
- 17 For voltage shunt feedback amplifier input resistance
- (A) Decreases
 - (B) Becomes zero
 - (C) None
 - (D) Increases

- 18 Voltage shunt feedback amplifier is a
- (A) Pure current amplifier
 - (B) Transconductance amplifier
 - (C) Transresistance amplifier
 - (D) Pure voltage amplifier
- 19 Select the correct relation for CE configuration
- (A) $I_b = h_{ie}I_b + h_{re}V_c$, $V_c = h_{fe}I_b + h_{oe}V_c$
 - (B) $V_e = h_{ie}I_c + h_{re}V_c$, $I_c = h_{fe}I_c + h_{oe}V_b$
 - (C) $V_c = h_{ie}I_b - h_{re}V_c$, $I_b = h_{fe}I_c - h_{oe}V_c$
 - (D) $V_b = h_{ie}I_b + h_{re}V_c$, $I_c = h_{fe}I_b + h_{oe}V_c$
- 20 h_{fe} is
- (A) A negative number
 - (B) Zero
 - (C) All of these
 - (D) A positive number
- 21 What is the general equation for voltage gain of an amplifier with feedback?
- (A) $A/(1+A\beta)$
 - (B) $A(1-A\beta)$
 - (C) $A(1+A\beta)$
 - (D) $A/(1-A\beta)$
- 22 An amplifier has a voltage gain of 40. Calculate feedback in dB if a 10% negative feedback is introduced ?
- (A) -14 dB
 - (B) 1.4 dB
 - (C) -1.4 dB
 - (D) 14 dB

- 23 The frequency range of an audio amplifier is
- (A) 20 Hz to 20 kHz
 - (B) Few kHz to 100 MHz
 - (C) All of these
 - (D) 0 to few Hz
- 24 In class B amplifier the Q – point is located
- (A) Near the saturation region
 - (B) Near the cut off region
 - (C) Below the cut off region
 - (D) At the centre of the active region
- 25 An ideal current amplifier must have
- (A) Zero input resistance and zero output resistance
 - (B) Zero input resistance and infinite output resistance
 - (C) Infinite input resistance and infinite output resistance
 - (D) Infinite input resistance and zero output resistance

- 26 With negative feedback the bandwidth _____ and the noise _____.
- (A) increases, decreases
- (B) decreases, increases
- (C) decreases, decreases
- (D) increases, increases
- 27 If an amplifier has a bandwidth of 200 kHz and voltage gain of 50, what will be new bandwidth and gain if 5% negative feedback is introduced?
- (A) 7 kHz, 142.8
- (B) 70 kHz, 14.28
- (C) 700 Hz, 1.428
- (D) 0.7 MHz, 14.28
- 28 Design a voltage divider bias circuit for the following specifications
 $V_{cc} = 20 \text{ v}$, $I_c = 10 \text{ mA}$, $V_{CE} = 8 \text{ V}$, $\beta = 80$
- (A) $R_E = 200\text{k}\Omega$, $R_C = 1\Omega$, $R_2 = 160\Omega$, $R_1 = 1\text{k}\Omega$
- (B) $R_E = 200\text{m}\Omega$, $R_C = 10 \text{ k}\Omega$, $R_2 = 16\Omega$, $R_1 = 1\text{k}\Omega$
- (C) $R_E = 20 \mu\Omega$, $R_C = 1 \text{ m}\Omega$, $R_2 = 1600\text{M}\Omega$, $R_1 = 10\text{k}\Omega$
- (D) $R_E = 200\Omega$, $R_C = 1 \text{ k}\Omega$, $R_2 = 1600\Omega$, $R_1 = 10\text{k}\Omega$