



- 1 What is the main advantage of CE amplifier over CB amplifier as far as biasing is concerned ?
- (A) None of these
  - (B) Single battery operation
  - (C) Small input resistance
  - (D) Less voltage gain
- 2 Which circuit is the best biasing circuit ?
- (A) Voltage divider bias with emitter bias
  - (B) Fixed bias circuit
  - (C) Emitter bias circuit
  - (D) Collector to base bias circuit
- 3 Input resistance for CB amplifier is
- (A) Greater than  $h_{ie}$
  - (B) Greater than  $h_{ib}$
  - (C) Less than  $h_{ib}$
  - (D) Equal to  $h_{ib}$
- 4 Power gain is always
- (A) All these
  - (B) A positive number
  - (C) A negative number
  - (D) Zero

- 5 Input resistance for CC amplifier is
- (A) None of these
  - (B) High
  - (C) Low
  - (D) Zero
- 6 The function of a transistor is to do \_\_\_\_\_.
- (A) Regulation
  - (B) Rectification
  - (C) Amplification
  - (D) Filtering
- 7 Stabilization means making \_\_\_\_\_ independent of temperature variations or variations of transistor parameters.
- (A) Collector Current
  - (B) Operating Point
  - (C) Supply Voltage
  - (D) Input Current
- 8 Which circuit has highest stability factor ?
- (A) Voltage divider bias with emitter bias
  - (B) Fixed bias circuit
  - (C) Emitter bias circuit
  - (D) Collector to base bias circuit

- 9 In the low frequency region of RC coupled amplifier the effect of capacitance is such that
- (A) The series capacitors and shunt capacitors are shorted
  - (B) The series capacitors are shorted
  - (C) Shunt capacitors are opened
  - (D) The series capacitors and shunt capacitors are opened
- 10 The half power frequency is also known as
- (A) All of these
  - (B) Cut off frequency
  - (C) Corner frequency
  - (D) Break frequency
- 11 What is the phase difference between input voltage and output voltage in a common emitter amplifier ?
- (A)  $90^\circ$
  - (B)  $180^\circ$
  - (C)  $-180^\circ$
  - (D) 0
- 12 For proper operation of transistor as an amplifier, (CE configuration) base emitter junction should be \_\_\_\_\_ and collector emitter junction should be \_\_\_\_\_.
- (A) (reverse biased, reverse biased)
  - (B) (reverse biased, forward biased)
  - (C) (forward biased, reverse biased)
  - (D) (forward biased, forward biased)

- 13 The circuit which exhibits 100% negative feedback
- (A) Emitter follower
  - (B) CE amplifier with bypass capacitor
  - (C) CE amplifier without bypass capacitor
  - (D) Collector to base biasing circuit
- 14 For voltage shunt feedback amplifier input resistance
- (A) None
  - (B) Increases
  - (C) Decreases
  - (D) Becomes zero
- 15 Voltage shunt feedback amplifier is a
- (A) Transresistance amplifier
  - (B) Pure voltage amplifier
  - (C) Pure current amplifier
  - (D) Transconductance amplifier
- 16 Select the correct relation for CE configuration
- (A)  $V_c = h_{ie}I_b - h_{re}V_c$  ,  $I_b = h_{fe}I_c - h_{oe}V_c$
  - (B)  $V_b = h_{ie}I_b + h_{re}V_c$  ,  $I_c = h_{fe}I_b + h_{oe}V_c$
  - (C)  $I_b = h_{ie}I_b + h_{re}V_c$  ,  $V_c = h_{fe}I_b + h_{oe}V_c$
  - (D)  $V_e = h_{ie}I_c + h_{re}V_c$  ,  $I_c = h_{fe}I_c + h_{oe}V_b$
- 17  $h_{fe}$  is
- (A) All of these
  - (B) A positive number
  - (C) A negative number
  - (D) Zero

- 18 What is the general equation for voltage gain of an amplifier with feedback?
- (A)  $A(1+A\beta)$
  - (B)  $A/(1-A\beta)$
  - (C)  $A/(1+A\beta)$
  - (D)  $A(1-A\beta)$
- 19 An amplifier has a voltage gain of 40. Calculate feedback in dB if a 10% negative feedback is introduced ?
- (A) -1.4 dB
  - (B) 14 dB
  - (C) -14 dB
  - (D) 1.4 dB
- 20 An amplifier has a voltage gain of 100. What will be the voltage gain if 10% negative feedback is given ?
- (A) 0.909
  - (B) 9.09
  - (C) 90%
  - (D) 90.0
- 21 An amplifier has a voltage gain of 40 and 200 kHz bandwidth. Calculate the bandwidth with feedback if a 10% negative feedback is introduced in series with input.
- (A) 500 kHz
  - (B) 100 kHz
  - (C) 10 kHz
  - (D) 1000 kHz
- 22 Example of voltage series negative feedback amplifier is
- (A) CB amplifier
  - (B) CE amplifier with bypass capacitor
  - (C) CE amplifier without bypass capacitor
  - (D) CC amplifier

- 23 In class B amplifier the Q – point is located
- (A) Below the cut off region
  - (B) At the centre of the active region
  - (C) Near the saturation region
  - (D) Near the cut off region
- 24 An ideal current amplifier must have
- (A) Infinite input resistance and infinite output resistance
  - (B) Infinite input resistance and zero output resistance
  - (C) Zero input resistance and zero output resistance
  - (D) Zero input resistance and infinite output resistance
- 25 With negative feedback the bandwidth \_\_\_\_\_ and the noise \_\_\_\_\_.
- (A) decreases, decreases
  - (B) increases, increases
  - (C) increases, decreases
  - (D) decreases, increases

- 26 If an amplifier has a bandwidth of 200 kHz and voltage gain of 50, what will be new bandwidth and gain if 5% negative feedback is introduced?
- (A) 700 Hz, 1.428
- (B) 0.7 MHz, 14.28
- (C) 7 kHz, 142.8
- (D) 70 kHz, 14.28
- 27 Design a voltage divider bias circuit for the following specifications  
 $V_{CC} = 20 \text{ V}$ ,  $I_C = 10 \text{ mA}$ ,  $V_{CE} = 8 \text{ V}$ ,  $\beta = 80$
- (A)  $R_E = 20 \mu\Omega$ ,  $R_C = 1 \text{ m}\Omega$ ,  $R_2 = 1600 \text{ M}\Omega$ ,  $R_1 = 10 \text{ k}\Omega$
- (B)  $R_E = 200 \Omega$ ,  $R_C = 1 \text{ k}\Omega$ ,  $R_2 = 1600 \Omega$ ,  $R_1 = 10 \text{ k}\Omega$
- (C)  $R_E = 200 \text{ k}\Omega$ ,  $R_C = 1 \Omega$ ,  $R_2 = 160 \Omega$ ,  $R_1 = 1 \text{ k}\Omega$
- (D)  $R_E = 200 \text{ m}\Omega$ ,  $R_C = 10 \text{ k}\Omega$ ,  $R_2 = 16 \Omega$ ,  $R_1 = 1 \text{ k}\Omega$
- 28 The frequency range of an audio amplifier is
- (A) All of these
- (B) 0 to few Hz
- (C) 20 Hz to 20 kHz
- (D) Few kHz to 100 MHz