



JB-3092
Second Year B. Sc. (Sem. III) Examination
March/April – 2013
Electronics : Paper - III
(Electronics Circuits & Applications)

Time : Hours]

[Total Marks : 50

Instructions :

(1)

<p>नीचे दर्शायेव निशानीवाणी विगतो उत्तरवही पर अवश्य कपवी. Fillup strictly the details of signs on your answer book.</p> <p>Name of the Examination : S. Y. B. SC. (SEM. 3)</p> <p>Name of the Subject : ELECTRONICS : PAPER - 3</p> <p>Subject Code No. : 3 0 9 2 Section No. (1, 2,.....): Nil</p>	<p>Seat No. : [][][][][][][]</p> <p>Student's Signature</p>
---	--

- (2) Draw neat and labeled diagrams wherever necessary
- (3) Assume and denote any data not provided
- (4) All symbols have their usual meaning

- 1 Answer in brief : 14
- (i) What is loop gain
 - (ii) Define Stability factor with reference to transistor biasing
 - (iii) Give the typical h-parameter values for CE amplifier configuration
 - (iv) The emitter follower circuit is having a unity gain why still it is called amplifier
- 2 (a) Discuss the Voltage divider bias with emitter bias circuit for stable transistor biasing 8
- (b) Briefly discuss bias compensation 4
- OR**
- 2 (a) Define the h-parameters. Discuss the simplified h-parameter model for CE configuration 8
- (b) Write the pair of equations representing the h-parameter equivalent model for all the three configurations 4

- 3 (a) Discuss the various types of feedbacks. Give a typical example of current shunt feedback 8
- (b) An amplifier with open loop gain of 50 is subject to a negative feedback of 20% calculate the resulting gain of the amplifier with feedback also predict the bandwidth of the amplifier with feedback if the open loop bandwidth is 1 MHz 4

OR

- 3 (a) Discuss the effect of the emitter bypass capacitor and coupling capacitor on lower cutoff frequency of the RC coupled amplifier 8
- (b) Define unity gain bandwidth and gain bandwidth product. 4
- 4 Write short notes : (any two) 12
- (i) Transformer coupled amplifier
- (ii) Black box theory
- (iii) Cause of instability in transistor biasing
- (iv) Effect of negative feedback on transistor amplifier performance