



JB-3161
Second Year B. Sc. (Sem. IV) Examination
April/May – 2013
Electronics : Paper - III
(Amplifiers and Linear Integrated Circuits)

Time : Hours]

[Total Marks :

Instructions :

(1)

<p>नीचे दशांशविक \leftarrow निशानीवाणी विगतो उत्तरवही पर अवश्य कपवी. Fillup strictly the details of \leftarrow signs on your answer book.</p> <p>Name of the Examination : <input type="text" value="S. Y. B. Sc. (Sem. 4)"/></p> <p>Name of the Subject : <input type="text" value="Electronics : Paper - 3"/></p> <p>Subject Code No. : <input type="text" value="3"/> <input type="text" value="1"/> <input type="text" value="6"/> <input type="text" value="1"/> Section No. (1, 2,.....) : <input type="text" value="Nil"/></p>	<p>Seat No. : <input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/></p> <div style="border: 1px solid black; border-radius: 15px; padding: 10px; text-align: center; width: 100%;">Student's Signature</div>
---	--

- (2) Question one is compulsory.
- (3) Assume data wherever necessary.
- (4) Draw neat circuit diagrams wherever necessary.

- 1 Write very short answers. 8
 - (1) What is cross over distortion ?
 - (2) What do you mean by positive feedback ?
 - (3) What are the requirements for oscillation ?
 - (4) Explain transistor as a switch.
 - (5) What is the amount of phase shift offered by each stage of RC circuit in Phase Shift Oscillator ?
 - (6) What is the use of speedup capacitor in bistable multivibrator ?
 - (7) Distinguish between Class A and Class B operation in amplifiers.
 - (8) What are the needs for tuned amplifier ?

- 2 (a) Derive the relation for the frequency of oscillation 10
and gain conditions for phase shift oscillator. Draw a neat diagram of a transistorized phase shift oscillator.

- (b) An RC phase shift oscillator has $R = 20k\Omega$ and $C = 0.01\mu F$. What is its frequency of oscillation ? 4

OR

- 2 (a) Explain the working principle of astable multivibrator. Derive the relation for frequency oscillation. Draw the diagram of a output waveforms. 8
- (b) Design an astable multivibrator to generate a square wave of frequency 2kHz. $V_{cc} = 15V, I_{csat} = 5 mA$ and $h_{fe\min} = 20$ 6
- 3 (a) Show that even harmonics are cancelled in push-pull amplifier. Discuss the Class-AB push-pull amplifier. 10
- (b) Prove that the power efficiency of a resistive load power amplifier is 25% while that of a transformer coupled power amplifier is 50%. 4

OR

- 3 (a) Explain the negative resistance oscillator. 10
- (b) Find out the frequency of the saw tooth wave form in a UJT oscillator with $R = 5k\Omega, C = 1\mu F$ and $\eta = 0.5$. 4
- 4 Write short notes. (any two) 14
- (1) Complementary Symmetry power amplifier
 - (2) LC oscillators.
 - (3) Monostable multivibrator.
 - (4) Difference amplifier.